

ECE 4200
Project 1 – MOSFET Characterization
Julio Ortiz Guzman
ECE4200_01

Summary

On the first page of your please summarize the results that you obtained in the following table

1)

Your name	Julio Ortiz Guzman
Wn1	9.90 μm
Wn2	17.30 μm
ron1 (when L = L1 and Vds = 2.5V)	89.77K
ron2 (when L = L2 and Vds = 2.5V)	330.357K
Wp1	15.60 μm
Wp2	27.15 μm
rop1 (when L = L1 and Vsd = 2.5V)	71.684K
rop2 (when L = L2 and Vsd = 2.5V)	238.252K

NMOS Characterization

2) NMOS calculations

Assume that $V_{\text{dsat}} = .25\text{V}$ for both transistors.

- Using your assigned current calculate Wn1. Round W up or down (whichever is more accurate) so that it a multiple of .15 μm . (Show your work in your report.)
- Using your assigned current calculate Wn2. Round W up or down (whichever is more accurate) so that it a multiple of .15 μm . (Show your work in your report)

Handwritten calculations for NMOS characterizations:

ECE 4200 Project 1
Given $I_D = 59 \mu\text{A}$ $L_1 = 0.6 \mu\text{m}$ $L_2 = 1.05 \mu\text{m}$
NMOS Calculations

$$I_D = \frac{\mu_n C_{ox}}{2} \frac{W_n}{L_n} (V_{gs} - V_{th})^2$$



$V_{\text{dsat}} = 0.25 \text{ V}$
 $\frac{\mu_n C_{ox}}{2} = 57.0 \mu\text{A/V}^2$

$$\frac{59 \cdot L_1}{\frac{\mu_n C_{ox}}{2} (V_{\text{dsat}}^2)} = W_{n1}$$
$$W_{n1} = \frac{59 \cdot 0.6}{57.0 (0.25^2)} = 9.937 \approx 9.90 \mu\text{m} = W_{n1}$$
$$W_{n2} = \frac{I_D \cdot L_2}{\frac{\mu_n C_{ox}}{2} (V_{\text{dsat}}^2)}$$
$$= \frac{59 \cdot 1.05}{57.0 (0.25^2)} = 17.389 \approx 17.45 \mu\text{m} = W_{n2}$$

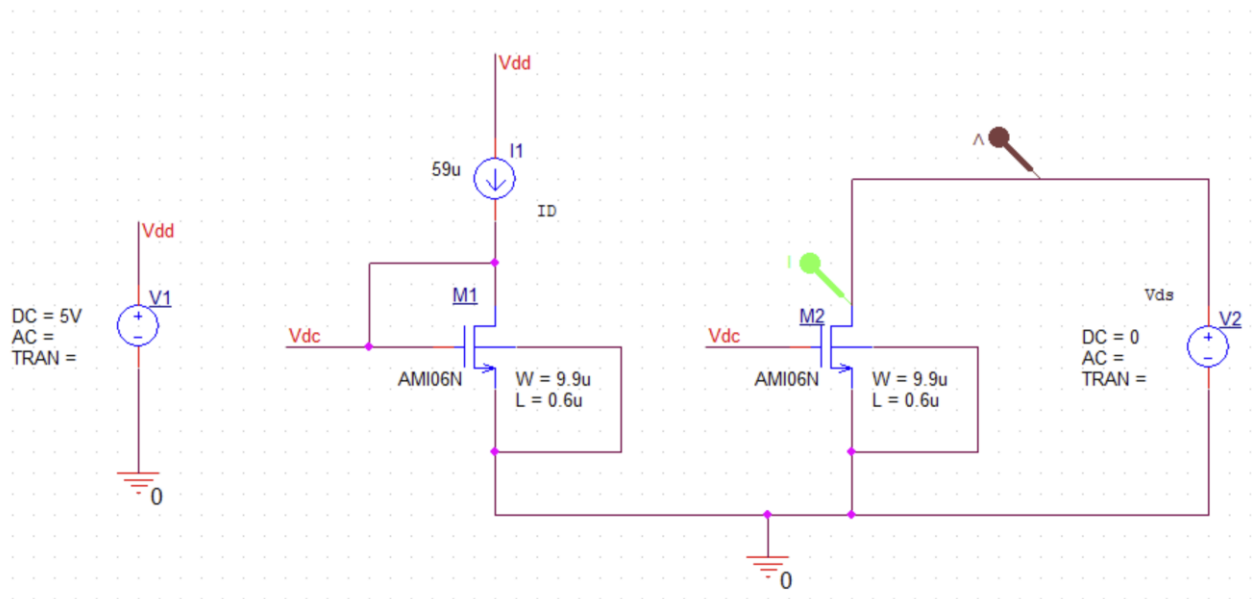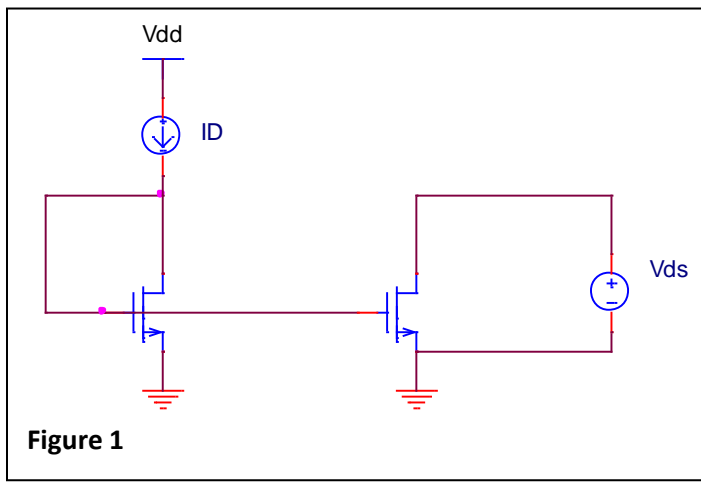3) NMOS characterization: ro for NMOS1 (short channel)


- Using transistor NMOS 1 and your assigned current construct the current mirror circuit shown in figure 1. Include a screen capture in your report.
 - Set V_{dd} to 5V

- Connect the body to the source, to eliminate body effect
- Use the value of I_D that has been assigned to you.
- Make sure transistor sizes and currents on your schematic are readable. (If necessary take a second screen shot and zoom in)



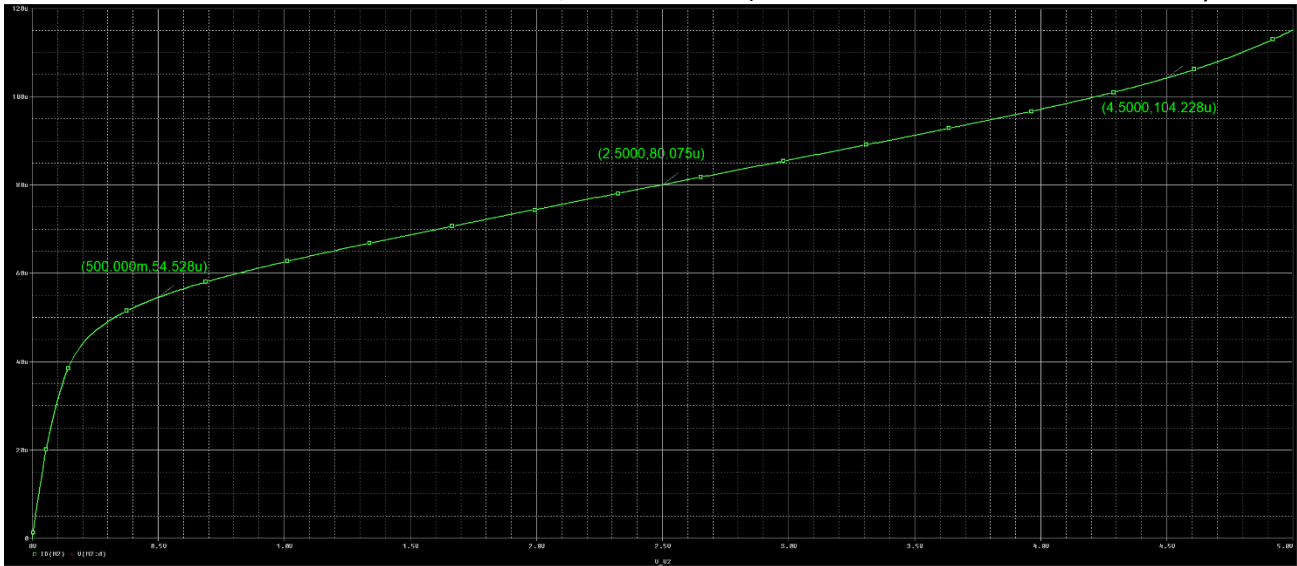
b) Plot I_D vs V_{ds} for V_{ds} ranging from 0 to 5V. Include a screen capture in your report.

- Measure the current when $V_{ds} = 0.5, 2.5V$ and $4.5V$ (use *trace cursors* or *markers* to show your work).



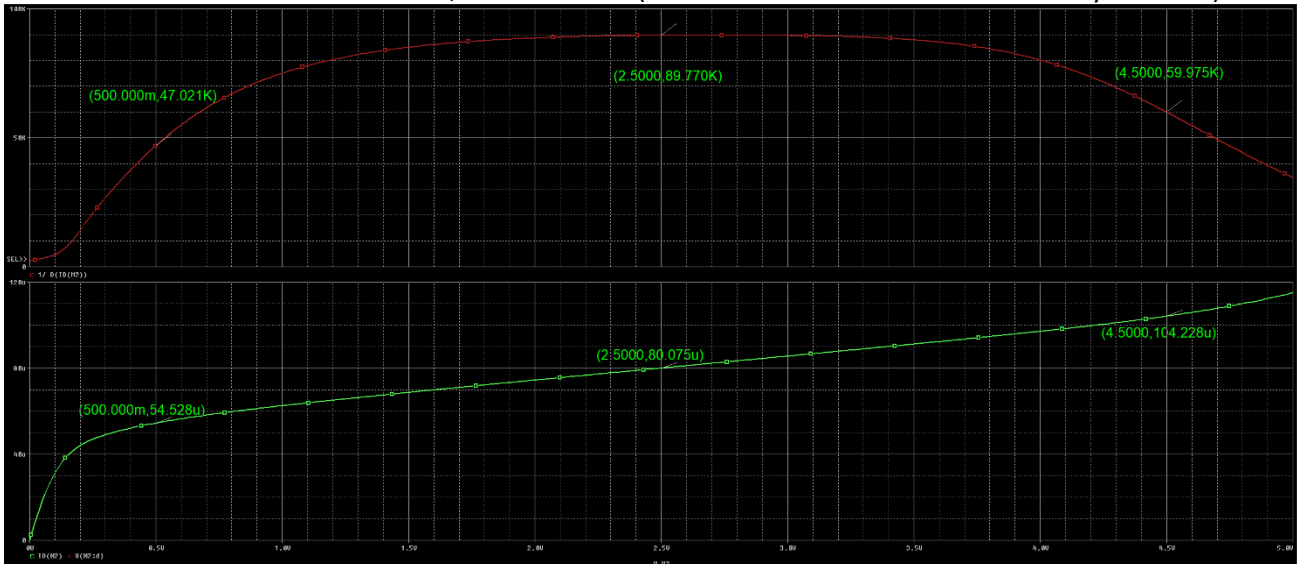c) Plot r_o vs V_{ds} for V_{ds} ranging from 0 to 5V. Include a screen capture in your report.

- Measure r_o when $V_{ds} = 0.5, 2.5V$ and $4.5V$ (use *trace cursors* or *markers* to show your work).




4) NMOS characterization: r_o for NMOS2 (long channel)

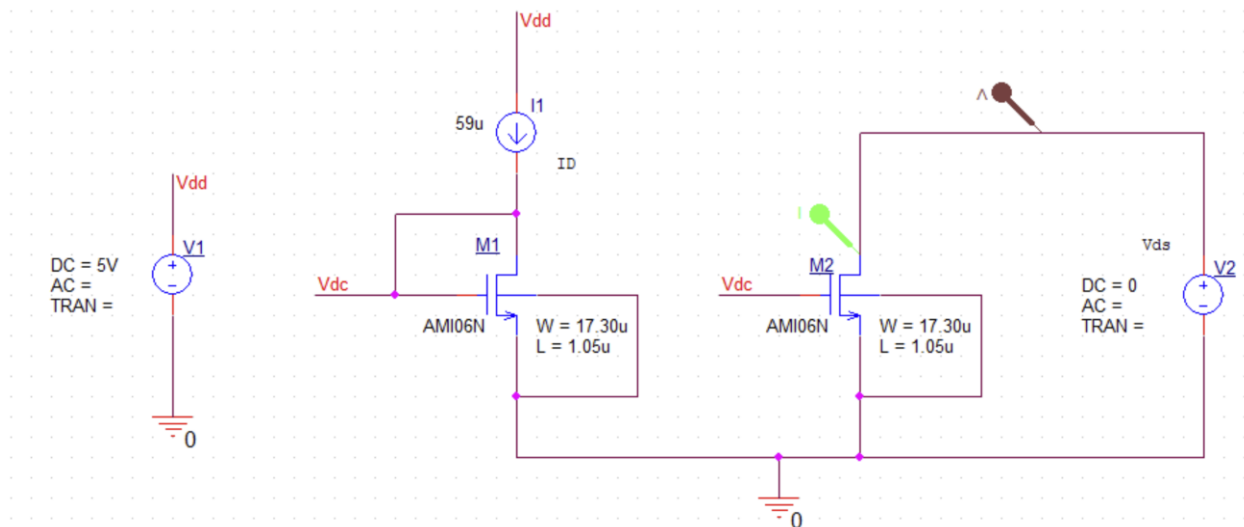a) Using transistor NMOS 2 and your assigned current construct the current mirror circuit shown in figure 1.


Include a screen capture in your report.

- Set V_{dd} to 5V
- Connect the body to the source, to eliminate body effect
- Use the value of I_D that has been assigned to you.
- Make sure transistor sizes and currents on your schematic are readable. (If necessary take a second screen shot and zoom in)



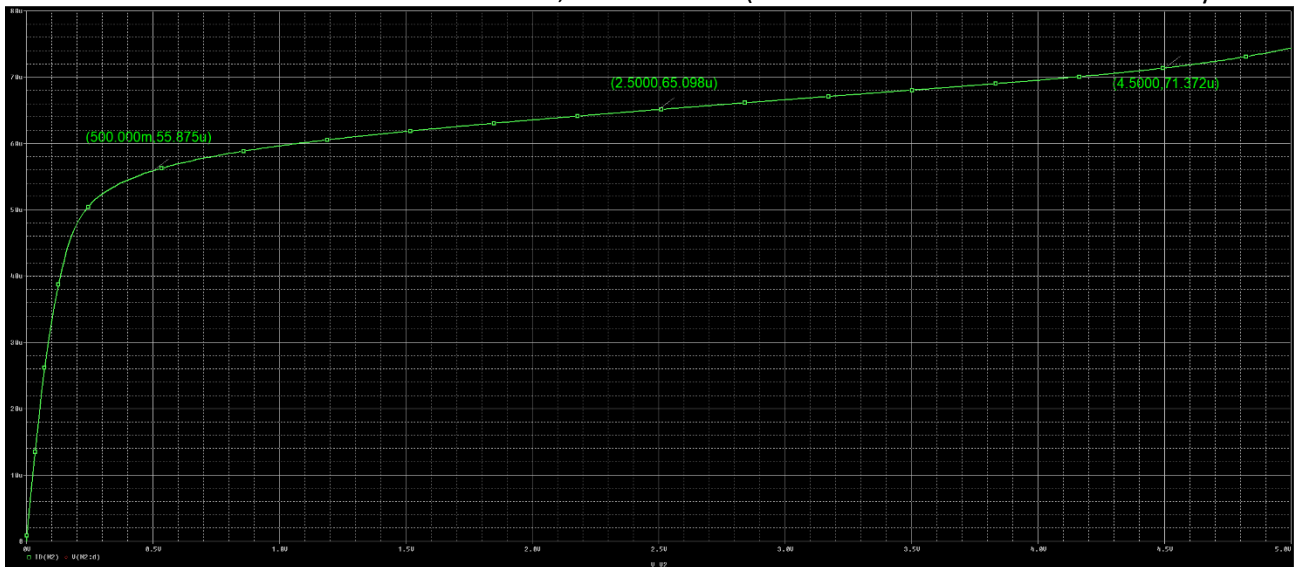
b) Plot I_D vs V_{ds} for V_{ds} ranging from 0 to 5V. Include a screen capture in your report.

- Measure the current when $V_{ds} = 0.5, 2.5V$ and $4.5V$ (use *trace cursors or markers* to show your work).



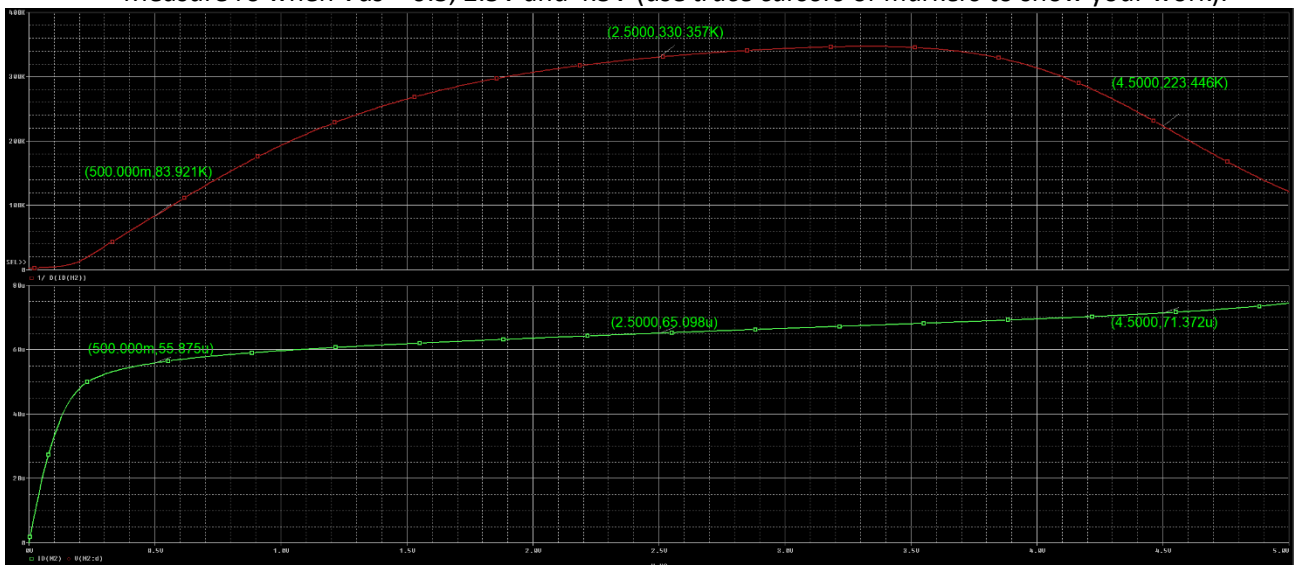c) Plot r_o vs V_{ds} for V_{ds} ranging from 0 to 5V. Include a screen capture in your report.

- Measure r_o when $V_{ds} = 0.5, 2.5V$ and $4.5V$ (use *trace cursors or markers* to show your work).



PMOS Characterization

5) PMOS calculations

Assume that $V_{dsat} = .35V$ for both transistors.

- Using your assigned current calculate W_{p1} . Round W up or down (whichever is more accurate) so that it is a multiple of $.15\mu m$. (show your work in your report)
- Using your assigned current calculate W_{p2} . Round W up or down (whichever is more accurate) so that it is a multiple of $.15\mu m$. (show your work in your report)

Handwritten calculations for PMOS:


$$I_D = \frac{\mu_p C_{ox}}{2} \frac{W_{p1}}{L_p} (V_{sg} + V_{TP})^2$$


Given: $V_{dsat} = 0.35$, $\frac{\mu_p C_{ox}}{2} = -18.6 \mu A/V^2$

$$W_{p1} = \frac{I_D \cdot L_p}{\frac{\mu_p C_{ox}}{2} (V_{dsat})^2}$$
$$W_{p1} = \frac{59 \cdot 0.6}{-18.6 (0.35)^2} = 15.536 \approx 15.60 \mu m$$
$$W_{p2} = \frac{59 \cdot 1.05}{-18.6 (0.35)^2} = 27.189 \approx 27.15 \mu m$$

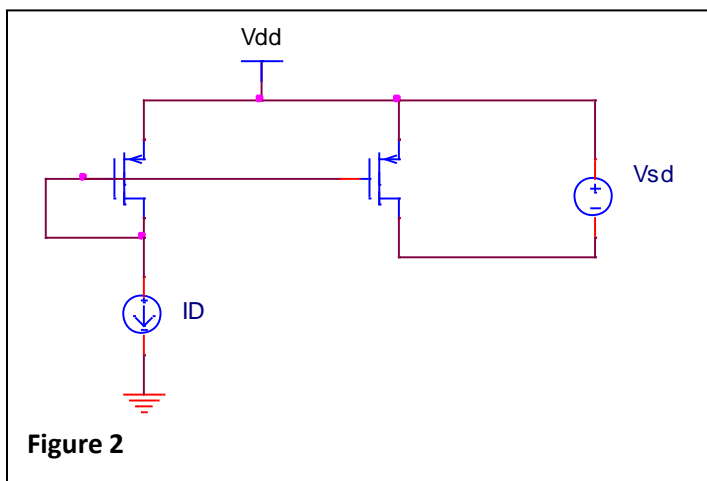6) PMOS characterization: r_o for PMOS1 (short channel)


- Construct the current mirror circuit shown in figure 2. Include a screen capture in your report.
 - Set V_{dd} to 5V
 - Connect the body to the source, to eliminate body effect
 - Use the value of I_D that has been assigned to you.
 - Make sure transistor sizes and currents on your schematic are readable. (If necessary take a second screen shot and zoom in)



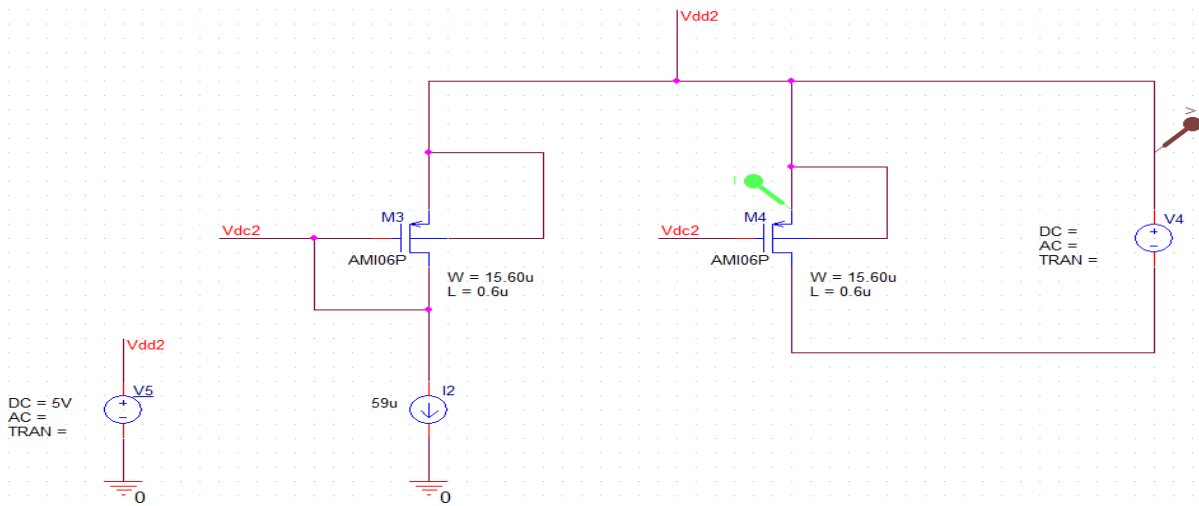

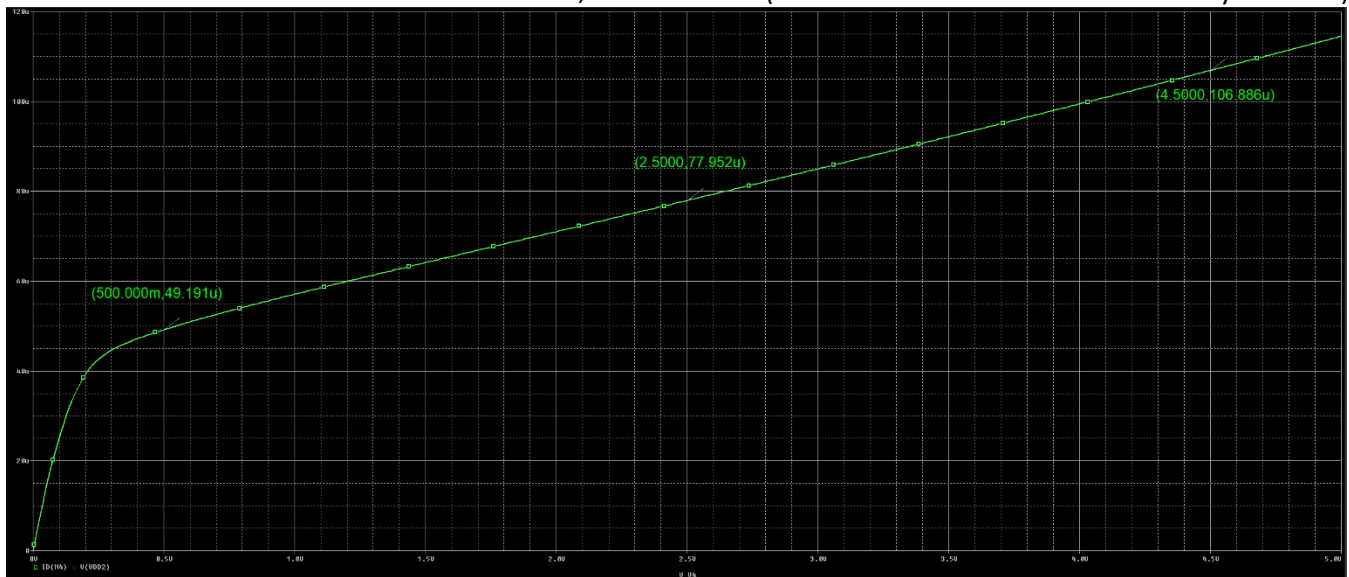
b) Plot ID vs Vsd for Vsd ranging from 0 to 5V include a screen capture in your report..

- Measure the current when Vsd =0.5, 2.5V and 4.5V (use *trace cursors* or *markers* to show your work).



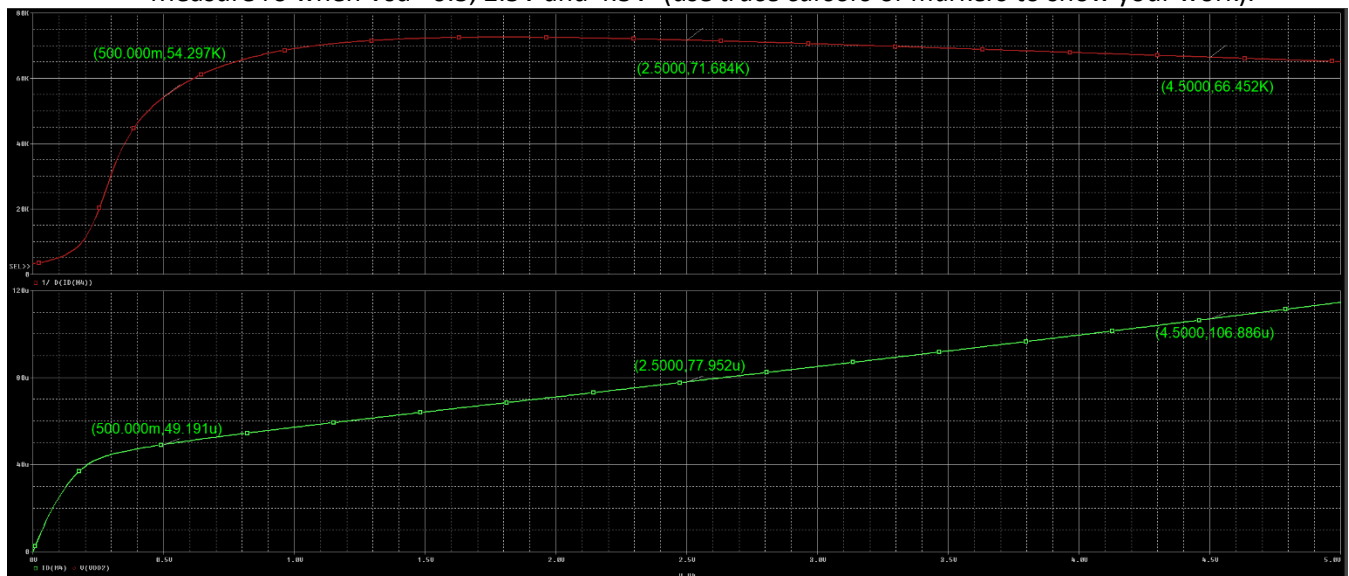c) Plot ro vs Vsd and take a screen capture.


- Measure ro when Vsd =0.5, 2.5V and 4.5V (use *trace cursors* or *markers* to show your work).



7) PMOS characterization: r_o for PMOS2 (long channel)

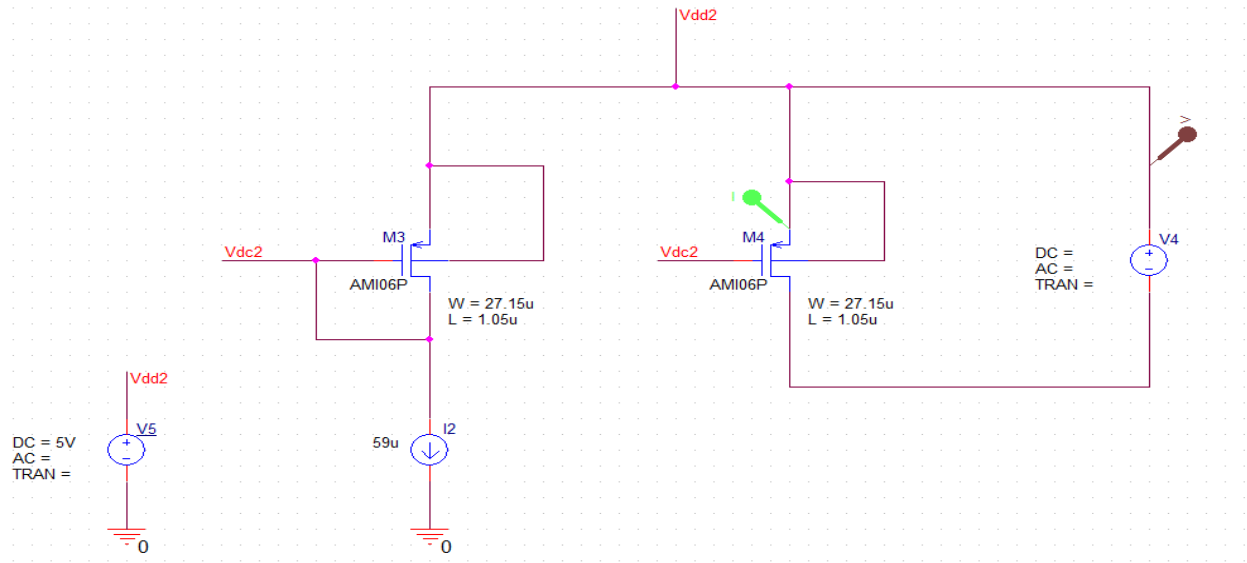
a) Construct the current mirror circuit shown in figure 2. Include a screen capture in your report.

- Set V_{dd} to 5V
- Connect the body to the source, to eliminate body effect
- Use the value of I_D that has been assigned to you.
- Make sure transistor sizes and currents on your schematic are readable. (If necessary take a second screen shot and zoom in)



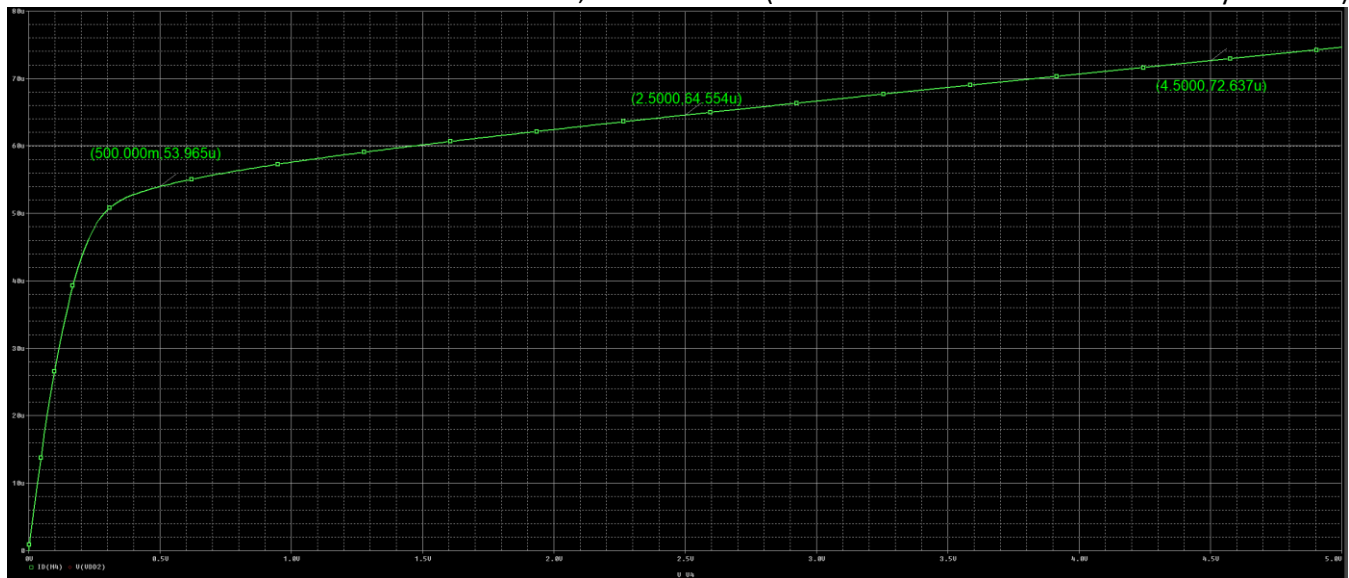
b) Plot I_D vs V_{sd} for V_{sd} ranging from 0 to 5V include a screen capture in your report..

- Measure the current when $V_{sd} = 0.5, 2.5V$ and $4.5V$ (use *trace cursors* or *markers* to show your work).



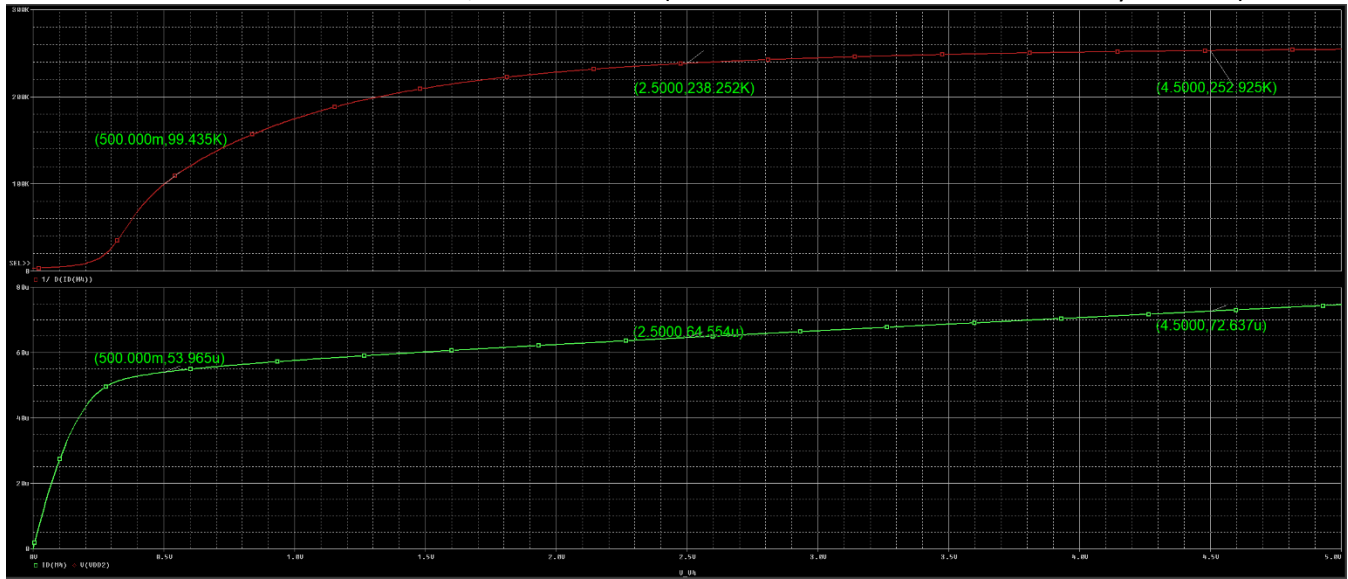c) Plot r_o vs V_{sd} and take a screen capture.

- Measure r_o when $V_{sd} = 0.5, 2.5V$ and $4.5V$ (use *trace cursors* or *markers* to show your work).



8) Conclusion

Briefly comment on the effect of V_{ds} , V_{sd} , and channel length on r_o . From your simulations is r_o larger for an NMOS or for a PMOS transistor?

As V_{ds} , V_{sd} and channel length increase r_o for both the NMOS and PMOS increase, however, for both lengths on the NMOS, when V_{ds} begins exceeding 3.5 volts, the resistance r_o starts to drop. Alternatively, the PMOS r_o stabilizes after approximately 2.5V. From the simulations we see that r_o is larger for an NMOS transistor.